

Issues when Grounding D.C. Coupled (Capless) Headphone Outputs

INTRODUCTION

In some situations, the headphone output of a product could be connected to another product, rather than headphones. In this situation it would appear that the “capless” (d.c. coupled) headphone mode, currently provided by the WM9711L, WM9712L, WM8750L, WM8751L and WM8955L, could not be used and large a.c. coupling capacitors would be needed instead. This application note looks at the issue of whether the output would be actually grounded by the connection or not, and therefore if a.c. coupling would be needed.

APPLICATION

AC-COUPLED HEADPHONE OUTPUT

The circuit diagram below shows how to connect a stereo headphone to the headphone output.

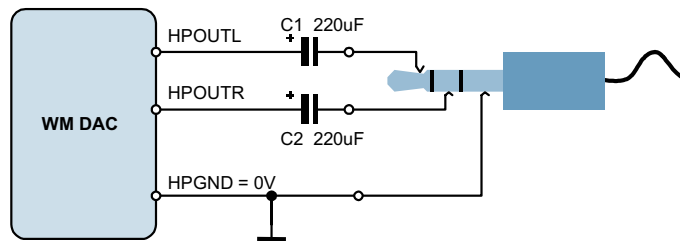


Figure 1 Simple Headphone Output Circuit Diagram

The DC blocking capacitors C1 and C2 together with the load resistance determine the lower cut-off frequency, f_c . Increasing the capacitance lowers f_c , improving the bass response. Smaller capacitance values will diminish the bass response. For example, with a 16 Ohm load and $C_1 = 220\mu\text{F}$:

$$f_c = 1 / 2\pi R_L C_1 = 1 / (2\pi \times 16\Omega \times 220\mu\text{F}) = 45 \text{ Hz}$$

DC COUPLED (CAPLESS) HEADPHONE OUTPUT

In the interest of saving board space and cost, it may be desirable to eliminate the $220\mu\text{F}$ DC blocking capacitors, with the added benefit of improved frequency response. This can be achieved by using OUT3 as a headphone pseudo-ground, as shown below.

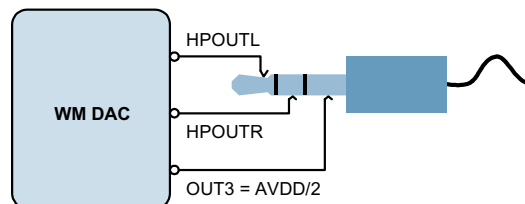


Figure 2 Capless Headphone Output Circuit Diagram

As the OUT3 pin produces a DC voltage of $AVDD/2$, there is no DC offset between HPOUTL/HPOUTR and OUT3, and therefore no DC blocking capacitors are required. However, this configuration has some drawbacks:

- The power consumption is increased, due to the additional power consumed in the OUT3 output buffer.
- If the DC coupled output is connected to the line-in of a grounded piece of equipment, then OUT3 becomes short-circuited. Although the thermal cut-out protection will prevent any damage to the IC, the audio signal will not be transmitted properly.

SOLUTIONS

HEADPHONE OUTPUT GROUND CASE 1

In the diagram below, the capless output is connected to a hi-fi amplifier, which is grounded. (This is only sometimes true.) In this case the DAC is powered by an isolated supply with no ground, like a typical plug-top PSU. Here it is acceptable to connect the headphone output to the amplifier, as there is no ground connection back to the DAC PSU to cause a short-circuit.

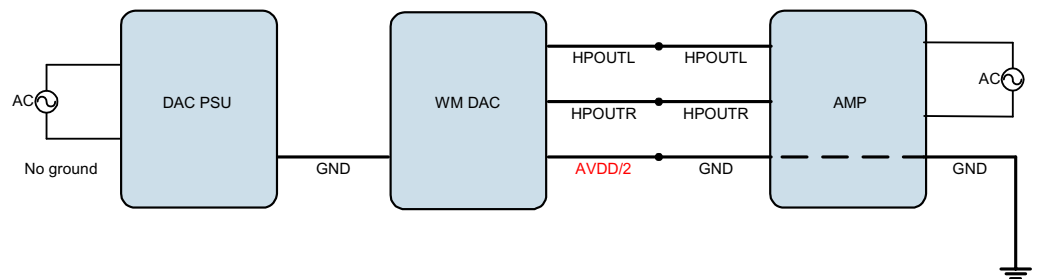


Figure 3 Acceptable Ground Connection 1

HEADPHONE OUTPUT GROUND CASE 2

In the diagram below, the capless output is connected to a mini PC amplifier, which is powered by an isolated supply with no ground, like a typical plug-top PSU. The DAC is inside a PC, which is grounded. In this case it is acceptable to connect the headphone output to the amplifier, as there is no ground connection back to the DAC PSU to cause a short-circuit.

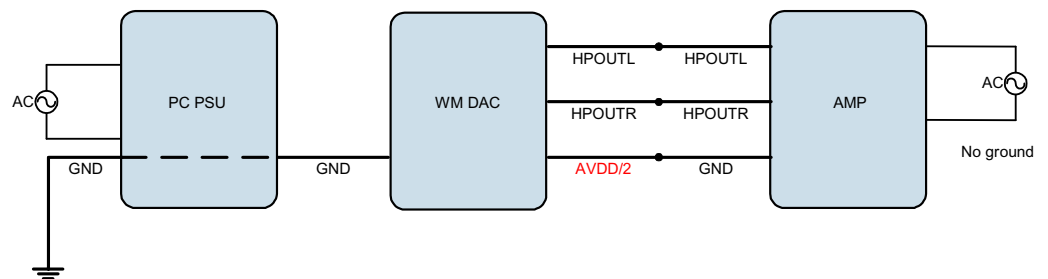


Figure 4 Acceptable Ground Connection 2

HEADPHONE OUTPUT GROUND CASE 3

In the diagram below, the capless output is connected to an amplifier, which is powered by a grounded supply. The DAC is inside a PC, which is also grounded. In this case it is *not* acceptable to connect the headphone output to the amplifier as there *is* a ground connection back to the DAC PSU, which will cause a short-circuit.

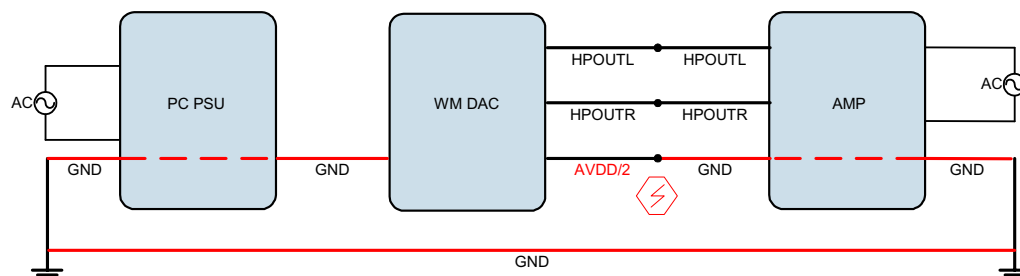


Figure 5 Bad Ground Connection 1

HEADPHONE OUTPUT GROUND CASE 4

In the diagram below, the capless output is connected to an amplifier, which is powered by a grounded supply. The DAC is inside a battery-powered CD player, which is grounded because it is powered by a non-isolated car charger. In this case it is *not* acceptable to connect the headphone output to the amplifier as there *is* a ground connection back to the DAC PSU, which will cause a short-circuit.

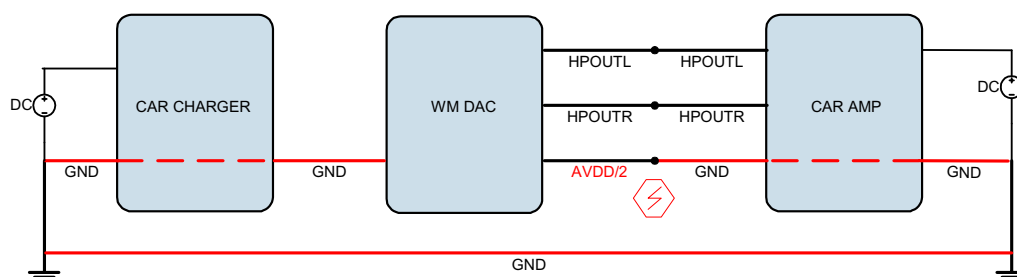


Figure 6 Bad Ground Connection 2

CONCLUSION

In most systems where the capless headphone output is used, it is safe to connect it to another piece of powered equipment, instead of headphones. In the rare case where both units are powered by a grounded supply, there will be a short-circuit, which will result in badly distorted sound output. In this case the thermal cut-out protection circuitry will stop any damage to the IC.

APPLICATION SUPPORT

If you require more information or require technical support please contact Wolfson Microelectronics Applications group through the following channels:

Email: apps@wolfsonmicro.com
 Telephone: +44 (0)131 272 7070
 Fax: +44 (0)131 272 7001
 Mail: Applications at the address on last page.

or contact your local Wolfson representative.

Additional information may be made available from time to time on our web site at <http://www.wolfsonmicro.com>

IMPORTANT NOTICE

Wolfson Microelectronics plc (WM) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current. All products are sold subject to the WM terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

WM warrants performance of its products to the specifications applicable at the time of sale in accordance with WM's standard warranty. Testing and other quality control techniques are utilised to the extent WM deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

In order to minimise risks associated with customer applications, adequate design and operating safeguards must be used by the customer to minimise inherent or procedural hazards. Wolfson products are not authorised for use as critical components in life support devices or systems without the express written approval of an officer of the company. Life support devices or systems are devices or systems that are intended for surgical implant into the body, or support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided, can be reasonably expected to result in a significant injury to the user. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

WM assumes no liability for applications assistance or customer product design. WM does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of WM covering or relating to any combination, machine, or process in which such products or services might be or are used. WM's publication of information regarding any third party's products or services does not constitute WM's approval, license, warranty or endorsement thereof.

Reproduction of information from the WM web site or datasheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations and notices. Representation or reproduction of this information with alteration voids all warranties provided for an associated WM product or service, is an unfair and deceptive business practice, and WM is not responsible nor liable for any such use.

Resale of WM's products or services with statements different from or beyond the parameters stated by WM for that product or service voids all express and any implied warranties for the associated WM product or service, is an unfair and deceptive business practice, and WM is not responsible nor liable for any such use.

ADDRESS:

Wolfson Microelectronics plc
Westfield House
26 Westfield Road
Edinburgh
EH11 2QB
United Kingdom

Tel :: +44 (0)131 272 7000

Fax :: +44 (0)131 272 7001

Email :: sales@wolfsonmicro.com